

Lecture

- Last Time: Combinational Circuits



- Circuits → Boolean Algebra → Circuits
- Building up larger components
 - half and full adders
 - sum of products
- 1-bit → N-bit operations
- Binary Addition and Subtraction
- Binary Coded Decimal (BCD) Addition

- Today:

- On-Off Switch: Not Data, but a Control Line
- Decoders and Multiplexers
- 1-bit Arithmetic and Logic Unit (ALU)
- Schematic of the CPU
- Schematic of Main Memory


Data Lines and Control Lines

  - All lines (wires) carry either a 0 or a 1
 - In the XOR circuit, we perceive these values to be data
 - In other circuits, e.g., decoder, some lines are for control
- On-Off Switch:
 - Use to turn on or turn off circuits





Data Lines and Control Lines

 - All lines (wires) carry either a 0 or a 1
 - In the XOR circuit, we perceive these values to be data
 - In other circuits, e.g., decoder, some lines are for control
- On-Off Switch:
 - Use to turn on or turn off circuits
 - C is a control line, D is a data line






D	C	Output (and)
0	0 (Off)	0 (Off)
0	1 (On)	0
1	0 (Off)	0 (Off)
1	1 (On)	1

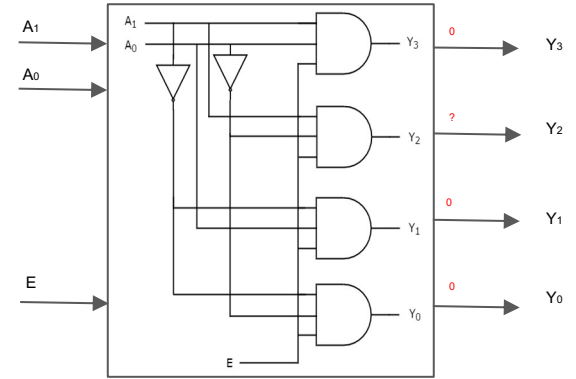 



Decoder Motivation

   - Consider a *two* 4-bit registers
- Use an On-Off switch to enable all the data lines from a register
 - C_0 and C_1 controls whether or not the register is selected



Decoder Motivation

 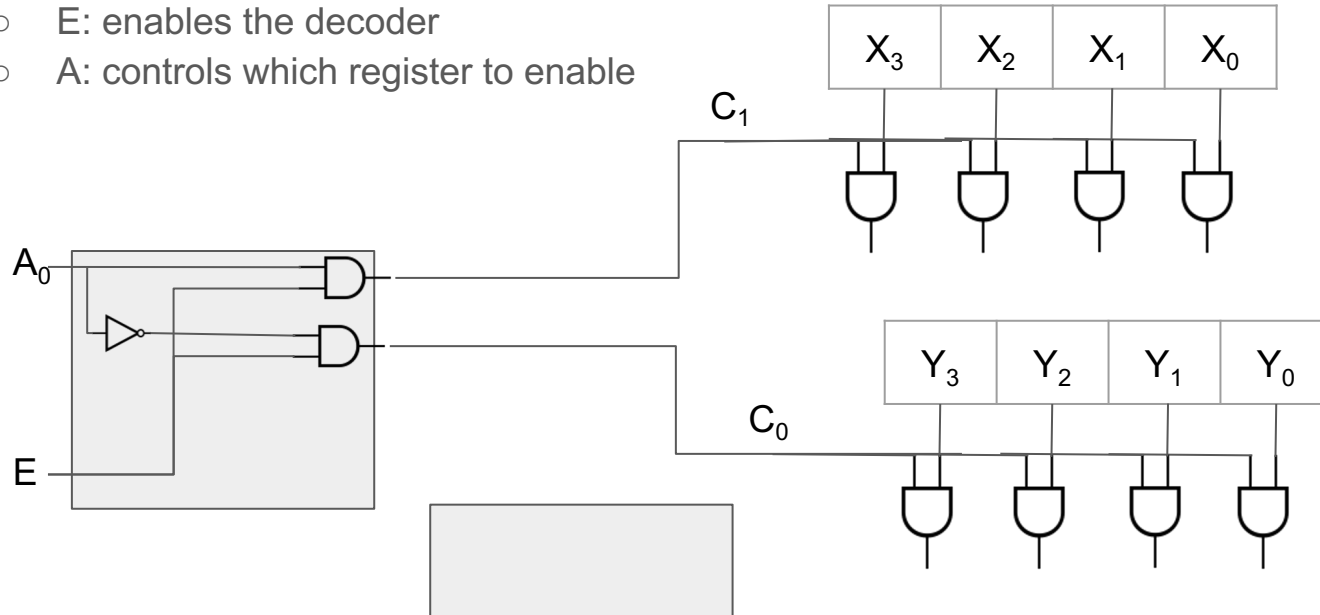
- Consider a *two* 4-bit registers
- Use an On-Off switch to enable all the data lines from a register
- Use 1-to-2 Decoder to select which register:
 - E: enables the decoder
 - A: controls which register to enable



Decoder: 2-to-4


- **N+1 Inputs:**
 - E: An "enable" line to active the circuit
 - A: Think of it as a binary number
- **2ⁿ Outputs:** A output line is set

E	A ₁	A ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	X	X	0	0	0	0
1	0	0				1
1	0	1			1	
1	1	0		1		
1	1	1	1			

 


Decoder: 2-to-4, 3-to-8, 4-to-16, 5-to-32

 - $N+1$ Inputs:
 - E: An "enable" line to active the circuit
 - A: Think of it as a binary number
- 2^n Outputs: A output line is set




E	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	X	X	0	0	0	0
1	0	0				1
1	0	1			1	
1	1	0		1		
1	1	1	1			

 

Decoder and Register Selection


- Consider a *two* 4-bit registers
 - Use an On-Off switch to enable all the data lines from a register
 - Use 1-to-2 Decoder to select which register:
 - E: enables the decoder
 - A: controls which register to enable
- | | | | |
|-------|-------|-------|-------|
| X_3 | X_2 | X_1 | X_0 |
|-------|-------|-------|-------|

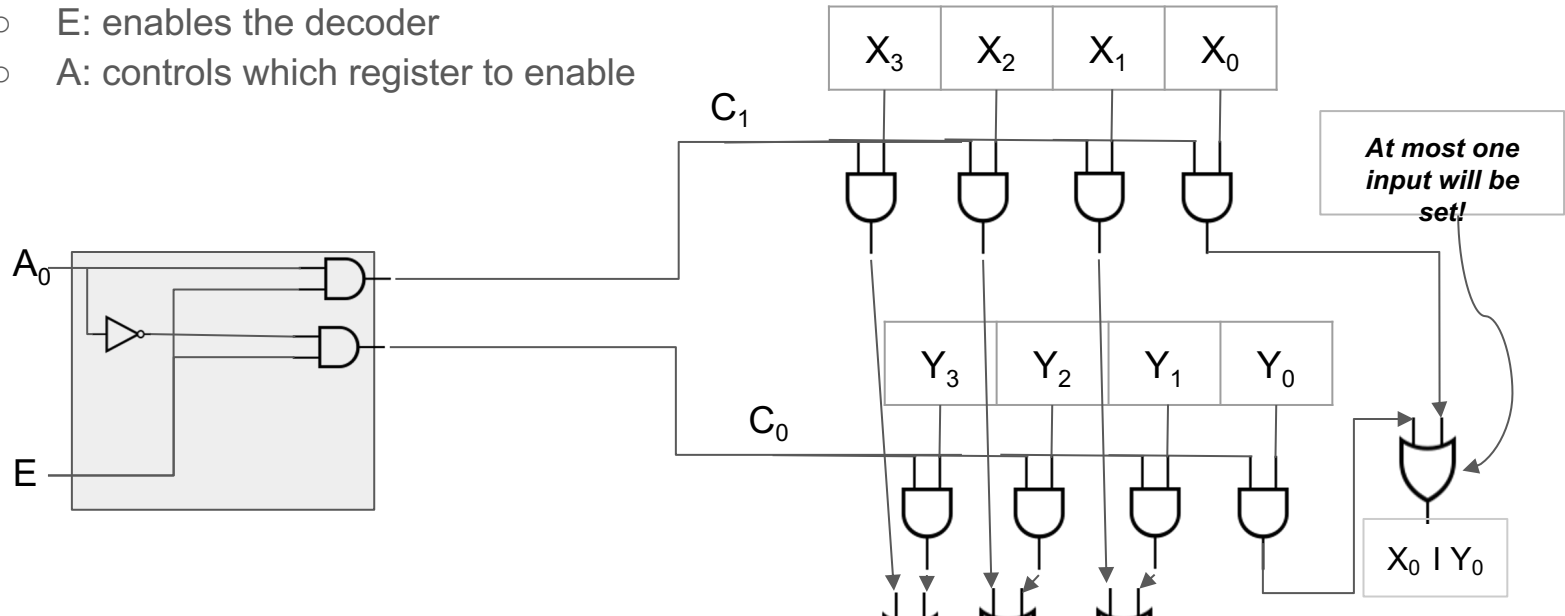

Eight 4-bit Register Bank

- $8 = 2^3$: Hence I need a 3-to-8 decoder
- Output to a single bus

5 == 101

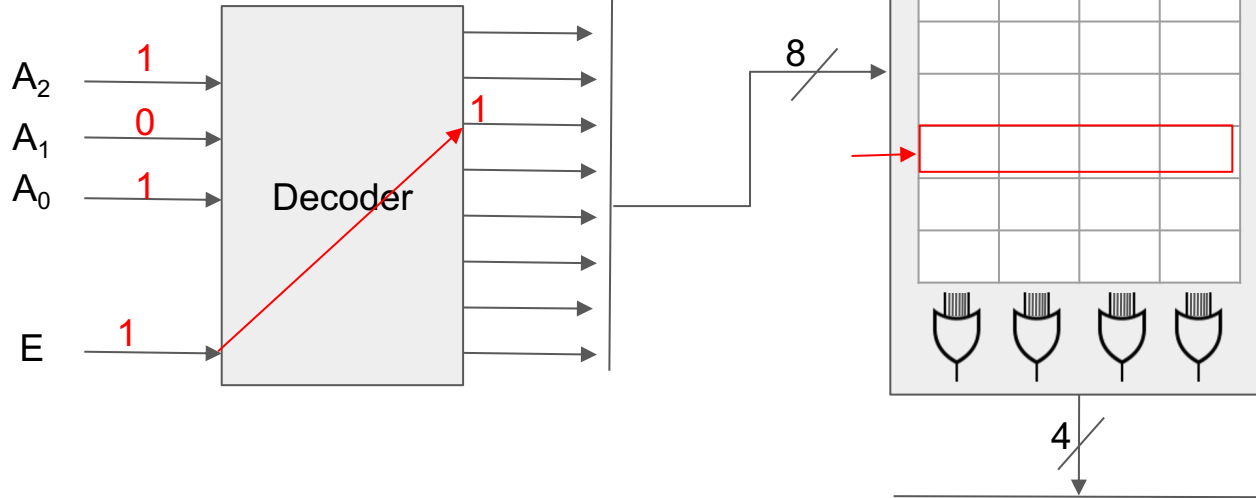


$$r7 = r1 + r4$$



Eight 4-bit Register Bank

- $8 = 2^3$: Hence I need a 3-to-8 decoder
- Provide for two data paths


1 == 001

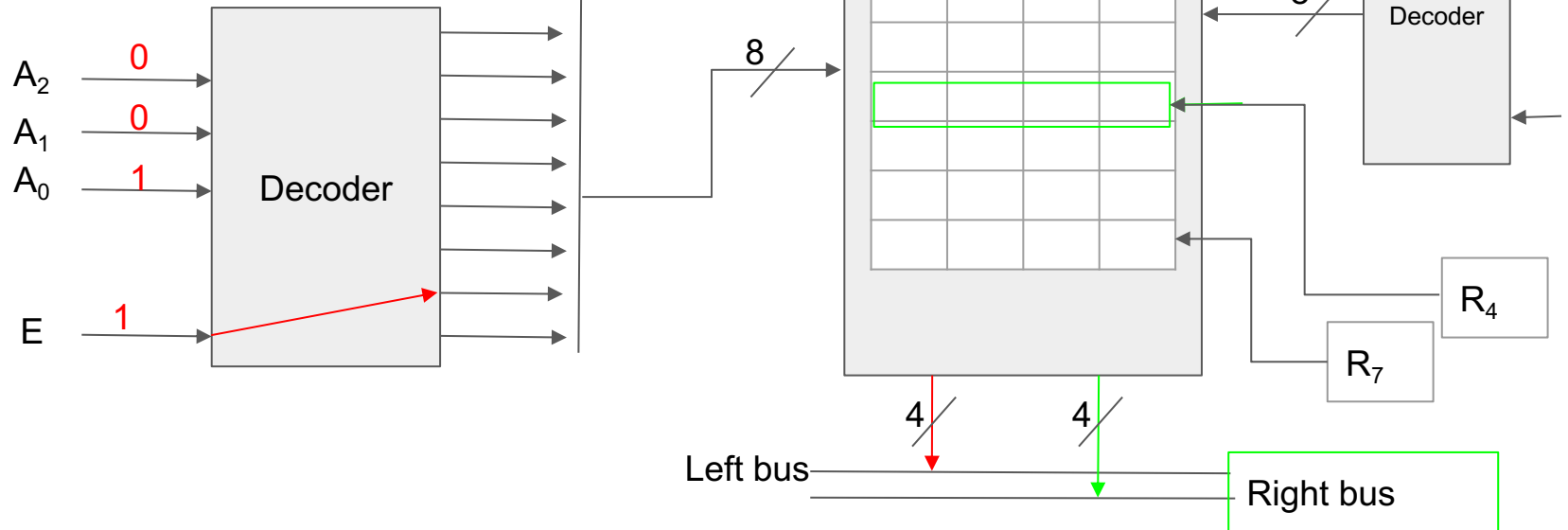

Two Data Paths: revisited

 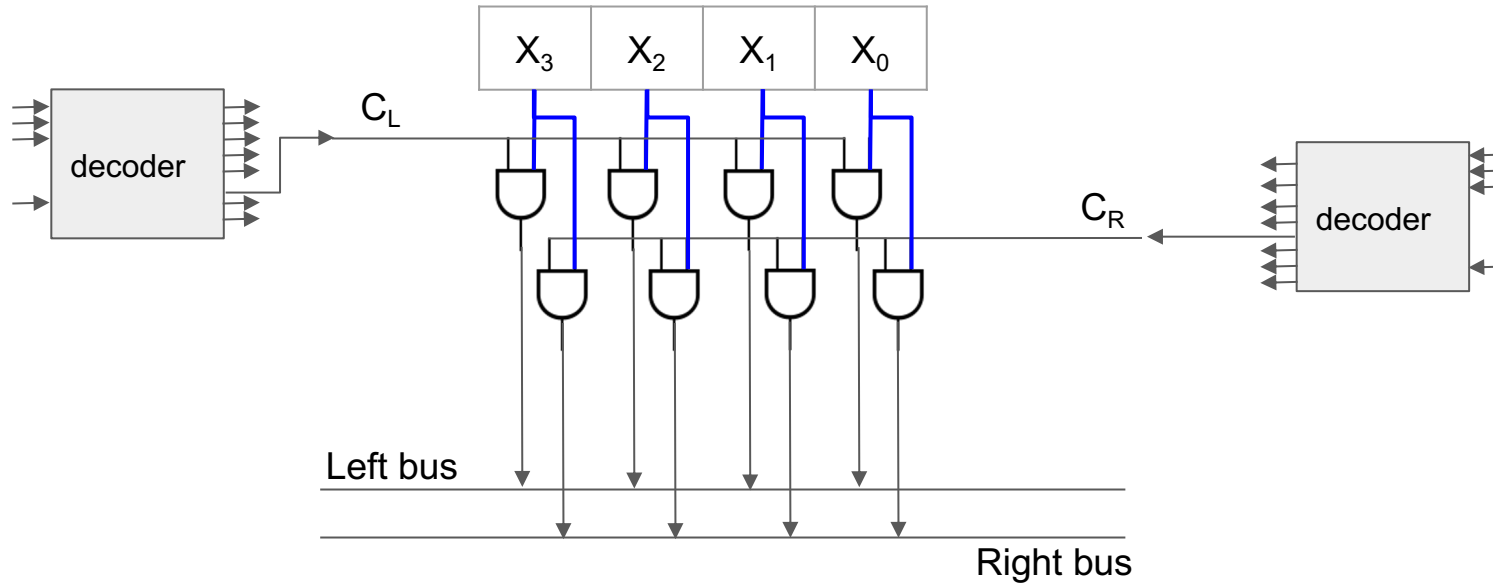


CPU: Almost!

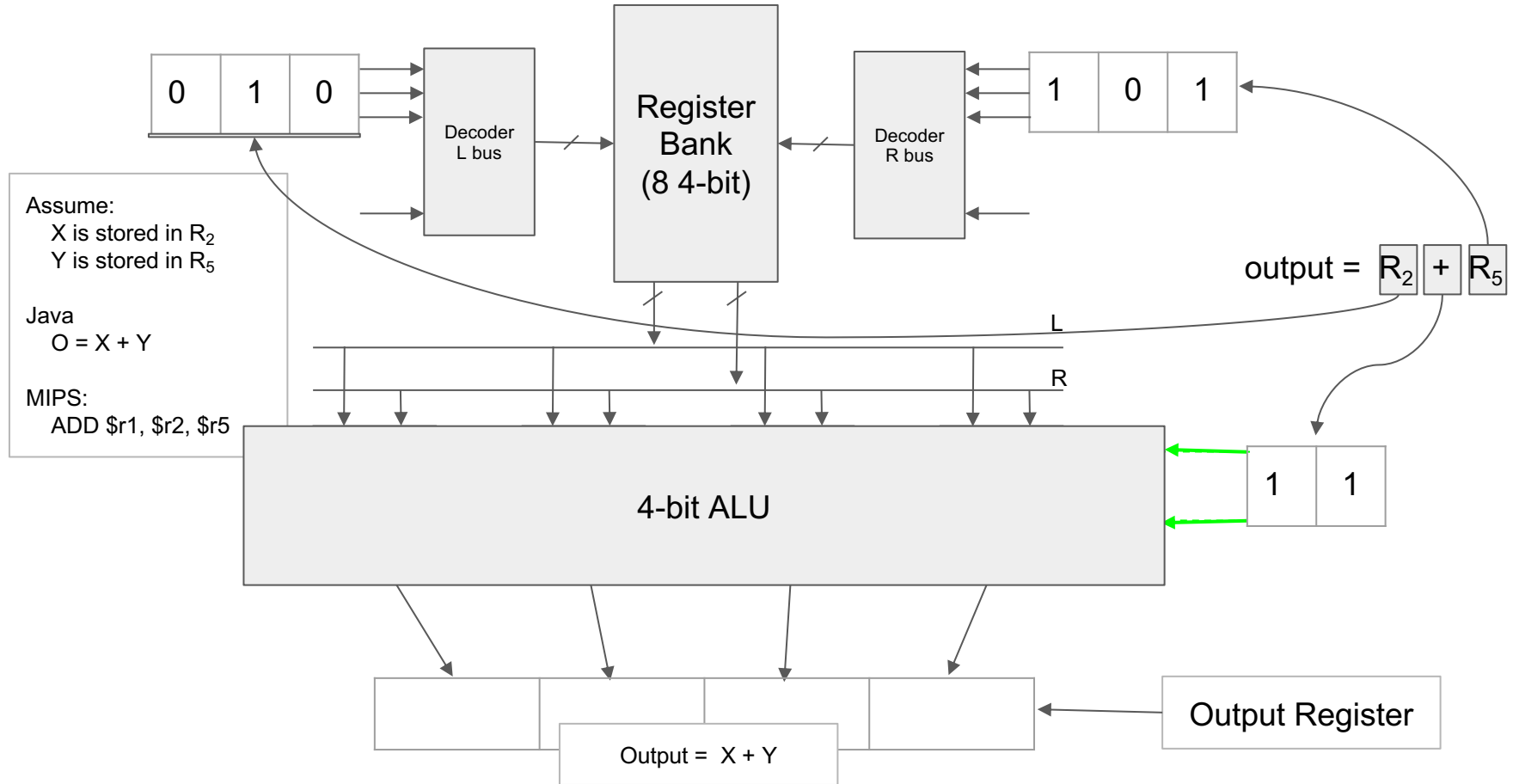

Arithmetic and Logical Unit (ALU)


- Let's build an 1-bit ALU with 4 possible functions:

- $X_0 + Y_0$: Binary Addition
- $X_0 \& Y_0$: Bitwise AND
- $X_0 | Y_0$: Bitwise OR
- $X_0 \wedge Y_0$: Bitwise XOR

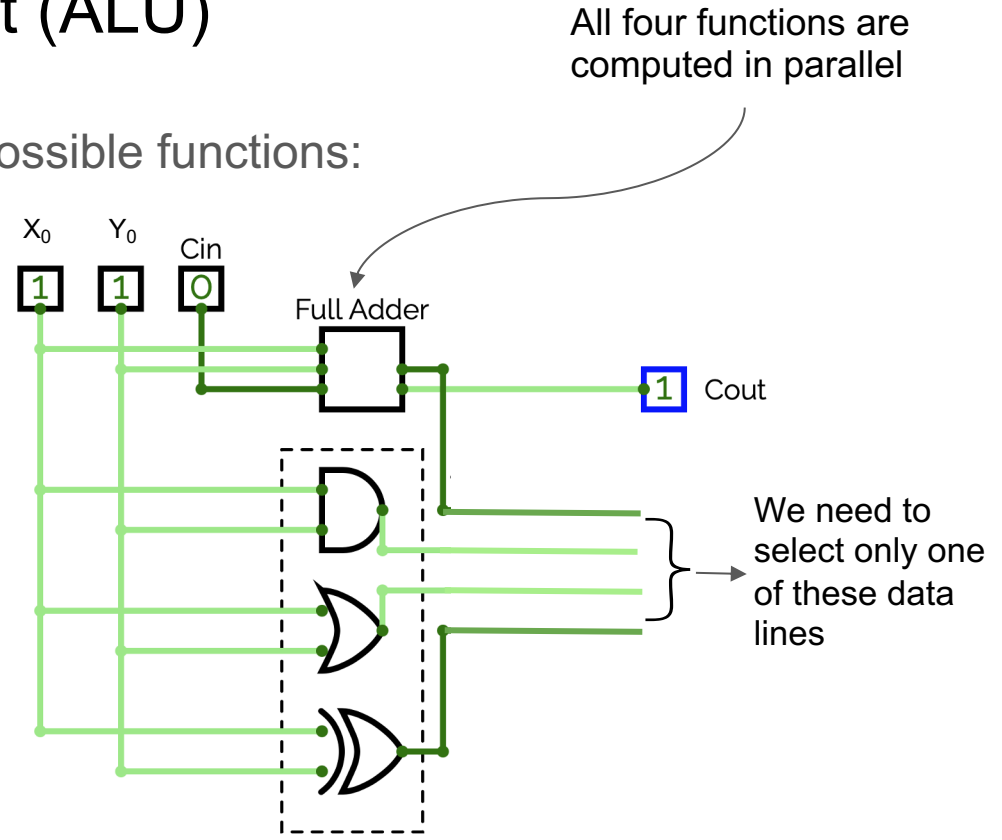

Multiplexer (Data Selector)

 - Inputs:
 - 2^N data input lines
 - N selector lines
- Outputs:
 - 1 dataline




S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

1-bit Arithmetic and Logical Unit (ALU)

All four functions are computed in parallel

- Let's build an 1-bit ALU with 4 possible functions:





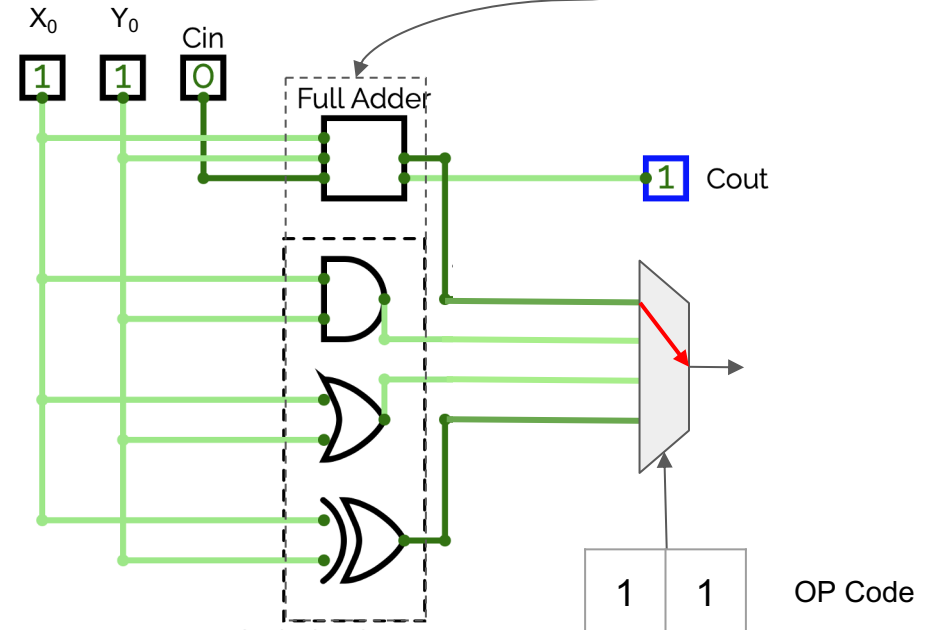
- $X_0 + Y_0$: (3) Binary Addition
- $X_0 \& Y_0$: (2) Bitwise And
- $X_0 \mid Y_0$: (1) Bitwise OR
- $X_0 \wedge Y_0$: (0) Bitwise XOR



Multiplexer for my ALU

- Inputs:
 - 2^N data input lines
 - N selector lines
- Outputs:
 - 1 dataline



Op	S ₁	S ₀	Y
^	0	0	I ₀
	0	1	I ₁
&	1	0	I ₂
+	1	1	I ₃

     


S₀

Multiplexer (Data Selector)

  - Inputs:
 - 2^N data input lines
 - N selector lines
- Outputs:
 - 1 dataline




CPU: Almost!

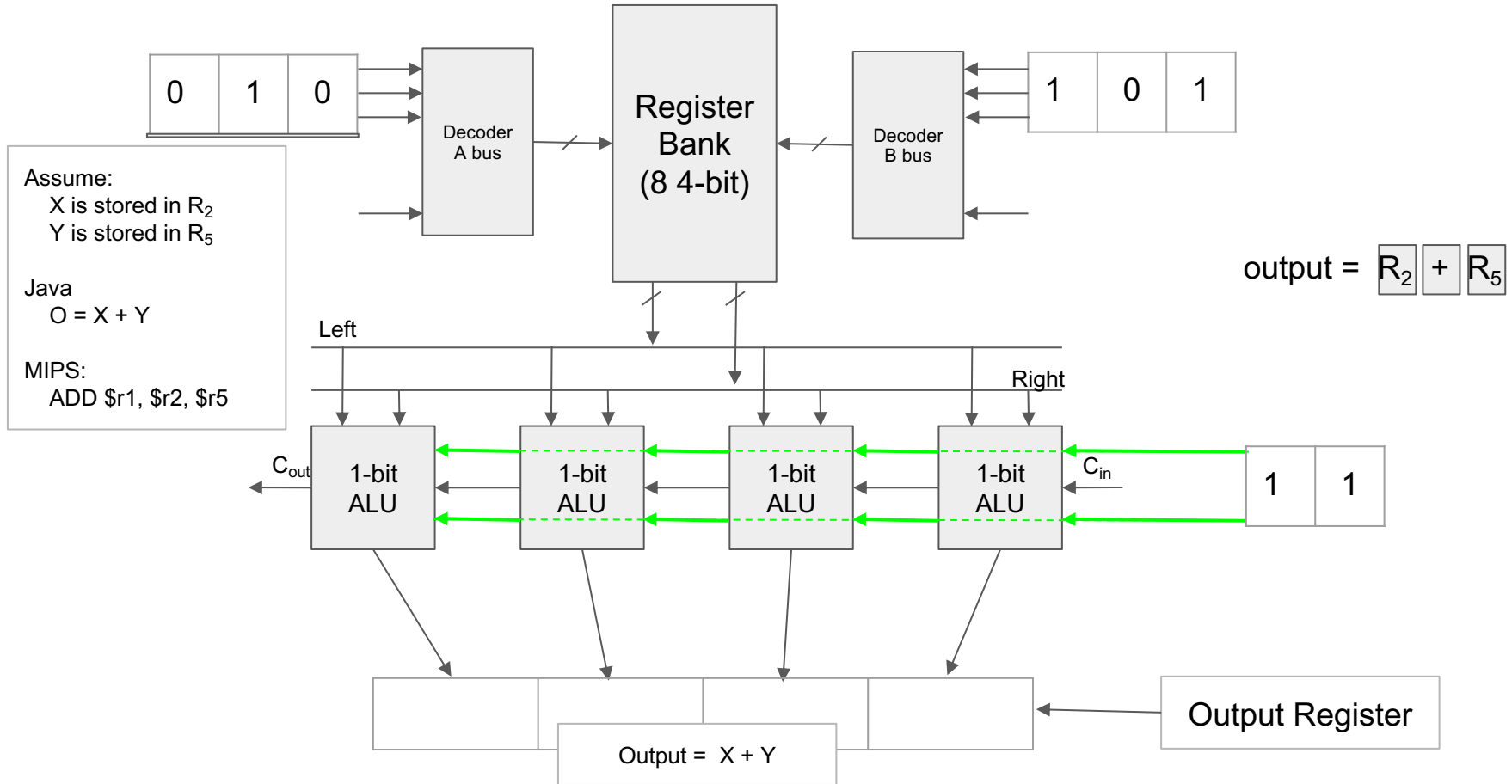

Schematic of Main Memory

- MBR: Memory Buffer Data Register

- The width of the data path

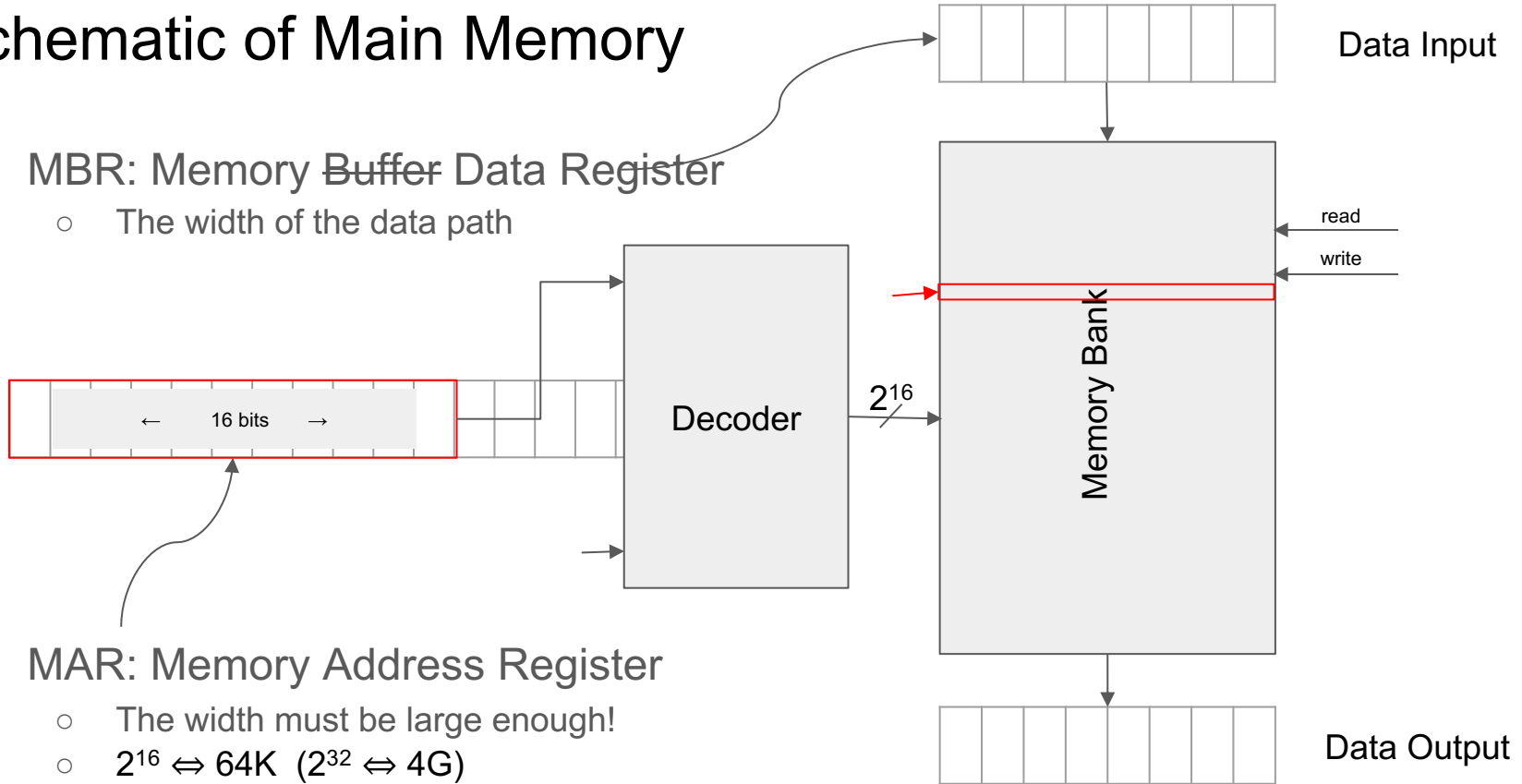


- MAR: Memory Address Register

- The width must be large enough!
- $2^{16} \Leftrightarrow 64K$ ($2^{32} \Leftrightarrow 4G$)

Other Memory Organizations

- Array of memory banks

- split into, say, 16 units

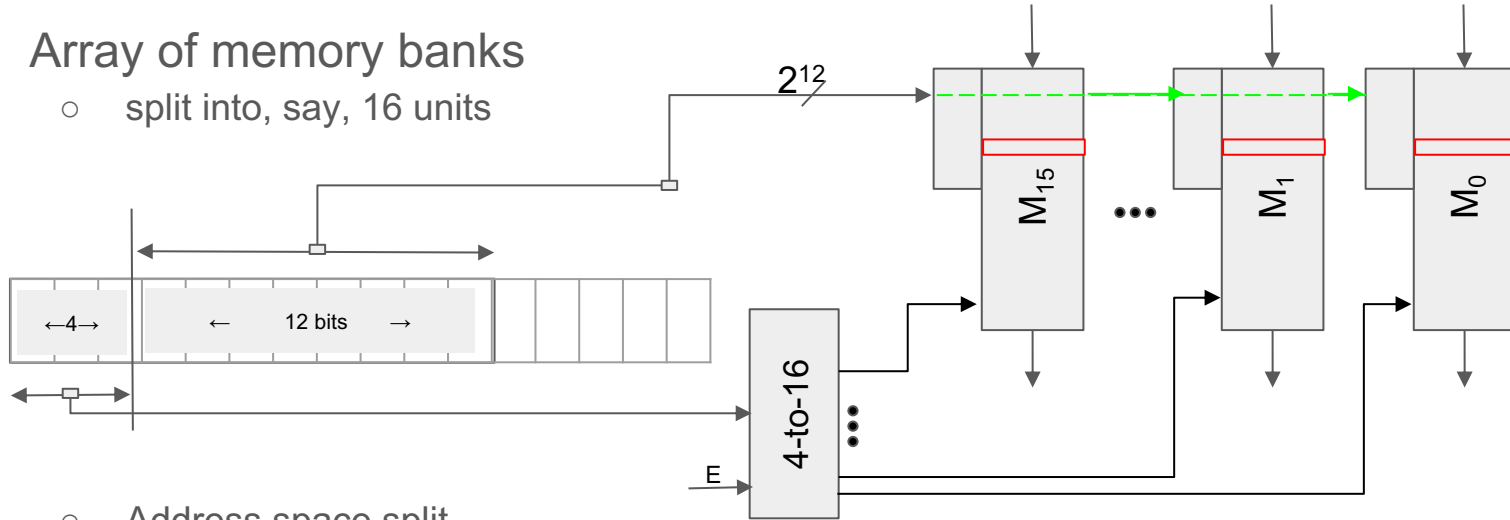

- Address space split

- 4 msb (most significant bits) determine which unit to use: a total of 4 bits : 15..12
- 12 lsb (least significant bits) provide the internal address: a total of 12 bits : 11..0